



ime in priimek:

vpisna št.:




Fakulteta za elektrotehniko, Univerza v Ljubljani

primeri števk: 0123456789

**1. test iz predmeta HAvOc (UNI)**

2.3.2011

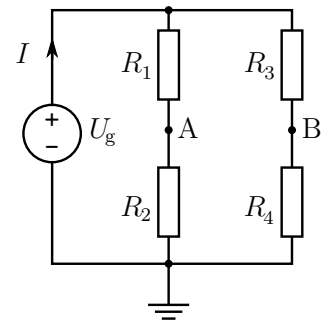1. Wheatstone bridge without null indicator has the following values of resistors:  $R_1 = 5 \Omega$ ,  $R_2 = 4 \Omega$ ,  $R_3 = 7 \Omega$  in  $R_4 = 4 \Omega$ . We have connected the bridge to a DC voltage source  $U = 1 \text{ V}$ .



- a) Determine the electric potential of junction B.

- (A)  $V_B \doteq 364 \text{ mV}$       (B)  $V_B = 5 \text{ V}$       (C)  $V_B \doteq 3.64 \text{ V}$       (D)  $V_B = 0 \text{ V}$


- b) What is the value of voltage  $U_{AB}$ ?

- (A)  $U_{AB} \doteq 80.8 \text{ mV}$       (B)  $U_{AB} \doteq 808 \text{ mV}$       (C)  $U_{AB} \doteq -80.8 \text{ mV}$       (D)  $U_{AB} = 333 \text{ mV}$

- c) Determine the current through resistor  $R_1$ .

- (A)  $I \doteq 111 \text{ mA}$       (B)  $I \doteq 208 \text{ mA}$       (C)  $I = 20 \text{ A}$       (D)  $I = 50 \text{ mA}$

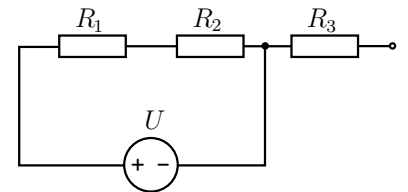2. The circuit is made of three resistors:  $R_1 = 5 \Omega$ ,  $R_2 = 2 \Omega$  in  $R_3 = 2 \Omega$ . Voltage source is  $U = 10 \text{ V}$ .



- a) What is the sum voltage on resistors  $R_1$  and  $R_2$ ?

- (A)  $U_{R_1+R_2} \doteq 2.86 \text{ V}$       (B)  $U_{R_1+R_2} = 35 \text{ V}$       (C)  $U_{R_1+R_2} = 5 \text{ V}$       (D)  $U_{R_1+R_2} = 10 \text{ V}$


- b) How much is the voltage on resistor  $R_3$ ?

- (A)  $U_{R_3} \doteq 2.86 \text{ V}$       (B)  $U_{R_3} = 0 \text{ V}$       (C)  $U_{R_3} = 10 \text{ V}$       (D)  $U_{R_3} = 5 \text{ V}$

- c) Determine the current through  $R_2$ !

- (A)  $I \doteq 1.43 \text{ A}$       (B)  $I = 20 \text{ A}$       (C)  $I \doteq 1.11 \text{ A}$       (D)  $I = 7.8 \text{ A}$

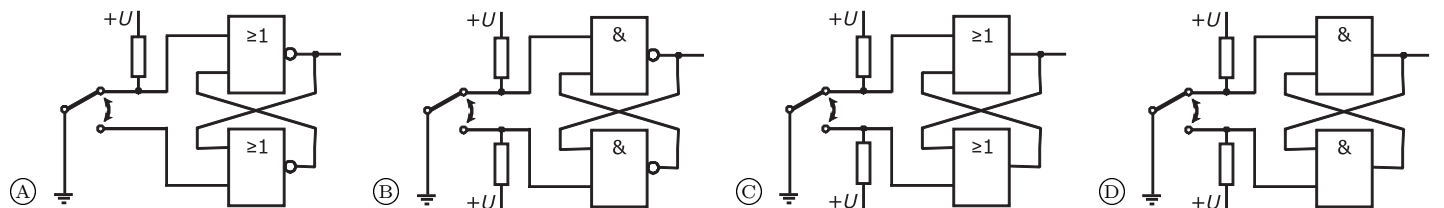3. Which circuits represents debounced switch?



4. The entropy of isolated thermodynamical system

- (A) can only decrease.      (B) is always zero.      (C) can only increase.      (D) is always positive constant.

This row can be used for further instructions.



ime in priimek:

vpisna št.:



Fakulteta za elektrotehniko, Univerza v Ljubljani


primeri števk: 0123456789

**1. test iz predmeta HAvOc (UNI)**

2.3.2011

1. The entropy of isolated thermodynamical system

- (A) is always positive constant. (B) is always zero. (C) can only decrease. (D) can only increase.

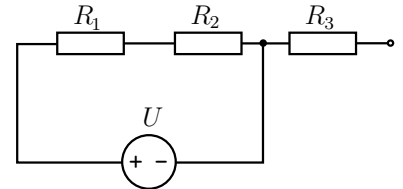2. The circuit is made of three resistors:  $R_1 = 10 \Omega$ ,  $R_2 = 2 \Omega$  in  $R_3 = 9 \Omega$ . Voltage source is  $U = 10 \text{ V}$ .a) What is the sum voltage on resistors  $R_1$  and  $R_2$ ?

- (A)  $U_{R_1+R_2} = 10 \text{ V}$  (B)  $U_{R_1+R_2} \doteq 13.3 \text{ V}$  (C)  $U_{R_1+R_2} = 120 \text{ V}$  (D)  $U_{R_1+R_2} = 20 \text{ V}$



b) How much is the voltage on resistor  $R_3$ ?

- (A)  $U_{R_3} \doteq 13.3 \text{ V}$  (B)  $U_{R_3} = 0 \text{ V}$  (C)  $U_{R_3} = 5 \text{ V}$  (D)  $U_{R_3} \doteq 1.11 \text{ V}$

c) Determine the current through  $R_2$ !

- (A)  $I \doteq 476 \text{ mA}$  (B)  $I = 7.8 \text{ A}$  (C)  $I = 1.3 \text{ A}$  (D)  $I \doteq 833 \text{ mA}$

3. Which circuits represents debounced switch?

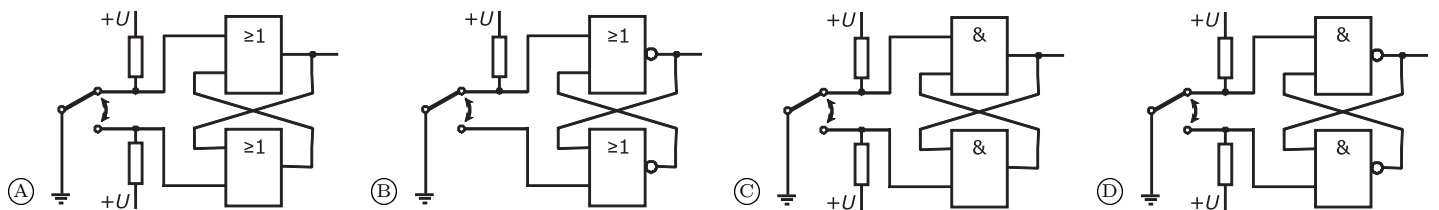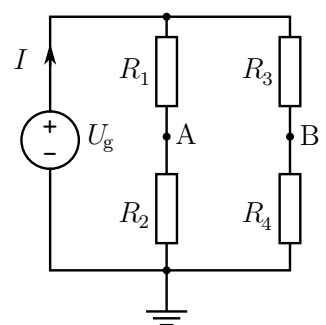4. Wheatstone bridge without null indicator has the following values of resistors:  $R_1 = 5 \Omega$ ,  $R_2 = 5 \Omega$ ,  $R_3 = 2 \Omega$  in  $R_4 = 3 \Omega$ . We have connected the bridge to a DC voltage source  $U = 1 \text{ V}$ .

a) Determine the electric potential of junction B.

- (A)  $V_B = 600 \text{ mV}$  (B)  $V_B = 6 \text{ V}$  (C)  $V_B = 500 \text{ mV}$  (D)  $V_B = 5 \text{ V}$

b) What is the value of voltage  $U_{AB}$ ?

- (A)  $U_{AB} = 333 \text{ mV}$  (B)  $U_{AB} = 500 \text{ mV}$  (C)  $U_{AB} = 250 \text{ mV}$  (D)  $U_{AB} = -100 \text{ mV}$

c) Determine the current through resistor  $R_1$ .

- (A)  $I = 15 \text{ A}$  (B)  $I \doteq 268 \text{ mA}$  (C)  $I = 300 \text{ mA}$  (D)  $I = 100 \text{ mA}$

This row can be used for further instructions.



ime in priimek:

vpisna št.:



Fakulteta za elektrotehniko, Univerza v Ljubljani

primeri števk: 0123456789


**1. test iz predmeta HAvOc (UNI)**

2.3.2011

**1. The entropy of isolated thermodynamical system**

- (A) is always zero. (B) is always positive constant. (C) can only decrease. (D) can only increase.

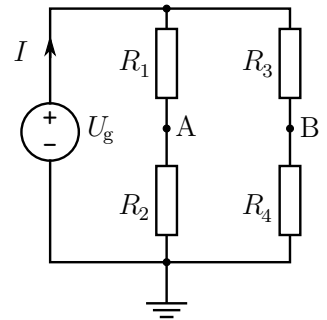2. Wheatstone bridge without null indicator has the following values of resistors:  $R_1 = 15 \Omega$ ,  $R_2 = 5 \Omega$ ,  $R_3 = 9 \Omega$  in  $R_4 = 4 \Omega$ . We have connected the bridge to a DC voltage source  $U = 1 \text{ V}$ .



- a) Determine the electric potential of junction B.

- (A)  $V_B = 5 \text{ V}$  (B)  $V_B \doteq 308 \text{ mV}$  (C)  $V_B = 1 \text{ V}$  (D)  $V_B \doteq 3.08 \text{ V}$


- b) What is the value of voltage  $U_{AB}$ ?

- (A)  $U_{AB} \doteq -57.7 \text{ mV}$  (B)  $U_{AB} \doteq 144 \text{ mV}$  (C)  $U_{AB} = 333 \text{ mV}$  (D)  $U_{AB} \doteq -442 \text{ mV}$

- c) Determine the current through resistor  $R_1$ .

- (A)  $I \doteq 153 \text{ mA}$  (B)  $I \doteq 127 \text{ mA}$  (C)  $I = 50 \text{ mA}$  (D)  $I = 33 \text{ A}$

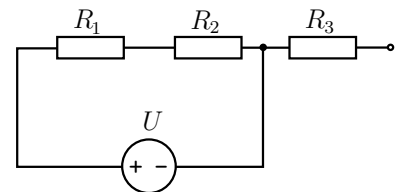3. The circuit is made of three resistors:  $R_1 = 10 \Omega$ ,  $R_2 = 4 \Omega$  in  $R_3 = 3 \Omega$ . Voltage source is  $U = 10 \text{ V}$ .



- a) What is the sum voltage on resistors  $R_1$  and  $R_2$ ?


- (A)  $U_{R_1+R_2} \doteq 46.7 \text{ V}$  (B)  $U_{R_1+R_2} = 20 \text{ V}$  (C)  $U_{R_1+R_2} = 10 \text{ V}$  (D)  $U_{R_1+R_2} \doteq 2.14 \text{ V}$

- b) How much is the voltage on resistor  $R_3$ ?

- (A)  $U_{R_3} \doteq 3.33 \text{ V}$  (B)  $U_{R_3} = 0 \text{ V}$  (C)  $U_{R_3} \doteq 2.14 \text{ V}$  (D)  $U_{R_3} \doteq 46.7 \text{ V}$

- c) Determine the current through  $R_2$ !

- (A)  $I = 30 \text{ A}$  (B)  $I \doteq 714 \text{ mA}$  (C)  $I = 1.3 \text{ A}$  (D)  $I = 7.8 \text{ A}$

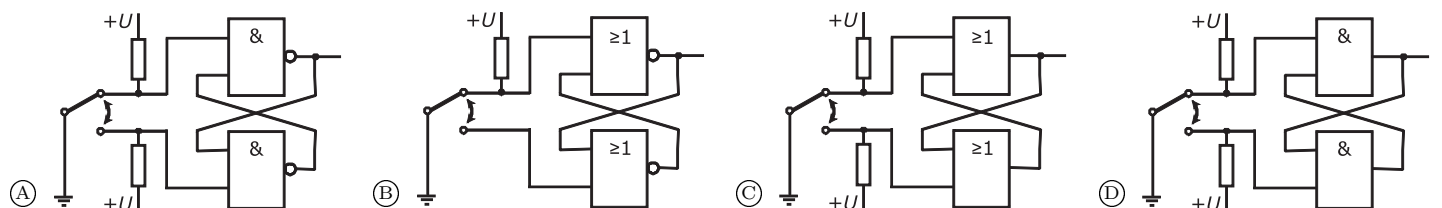**4. Which circuits represents debounced switch?**

This row can be used for further instructions.



ime in priimek:

vpisna št.:




Fakulteta za elektrotehniko, Univerza v Ljubljani

primeri števk: 0123456789

**1. test iz predmeta HAvOc (UNI)**

2.3.2011

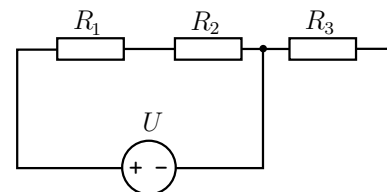1. The circuit is made of three resistors:  $R_1 = 5 \Omega$ ,  $R_2 = 3 \Omega$  in  $R_3 = 9 \Omega$ . Voltage source is  $U = 10 \text{ V}$ .



- a) What is the sum voltage on resistors  $R_1$  and  $R_2$ ?

- (A)  $U_{R_1+R_2} \doteq 8.89 \text{ V}$       (B)  $U_{R_1+R_2} = 80 \text{ V}$       (C)  $U_{R_1+R_2} \doteq 11.3 \text{ V}$       (D)  $U_{R_1+R_2} = 10 \text{ V}$


- b) How much is the voltage on resistor  $R_3$ ?

- (A)  $U_{R_3} \doteq 11.3 \text{ V}$       (B)  $U_{R_3} = 5 \text{ V}$       (C)  $U_{R_3} = 10 \text{ V}$       (D)  $U_{R_3} = 0 \text{ V}$

- c) Determine the current through  $R_2$ !

- (A)  $I = 0 \text{ A}$       (B)  $I = 7.8 \text{ A}$       (C)  $I = 1.25 \text{ A}$       (D)  $I = 90 \text{ A}$

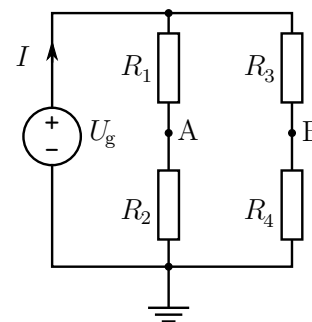2. Wheatstone bridge without null indicator has the following values of resistors:  $R_1 = 15 \Omega$ ,  $R_2 = 5 \Omega$ ,  $R_3 = 6 \Omega$  in  $R_4 = 6 \Omega$ . We have connected the bridge to a DC voltage source  $U = 1 \text{ V}$ .



- a) Determine the electric potential of junction B.

- (A)  $V_B = 500 \text{ mV}$       (B)  $V_B = 1.2 \text{ V}$       (C)  $V_B = 1 \text{ V}$       (D)  $V_B = 0 \text{ V}$

- b) What is the value of voltage  $U_{AB}$ ?

- (A)  $U_{AB} = -250 \text{ mV}$       (B)  $U_{AB} = 333 \text{ mV}$       (C)  $U_{AB} = 750 \text{ mV}$       (D)  $U_{AB} = 500 \text{ mV}$


- c) Determine the current through resistor  $R_1$ .

- (A)  $I = 50 \text{ mA}$       (B)  $I \doteq 31.3 \text{ mA}$       (C)  $I \doteq 133 \text{ mA}$       (D)  $I = 32 \text{ A}$

3. The entropy of isolated thermodynamical system

- (A) is always zero.      (B) is always positive constant.      (C) can only decrease.      (D) can only increase.

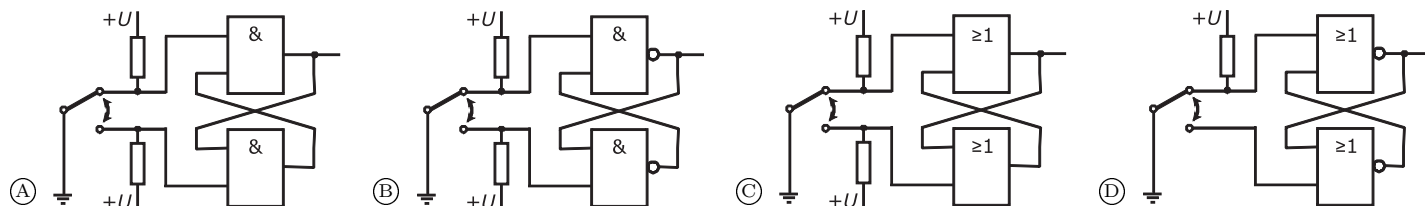4. Which circuits represents debounced switch?



This row can be used for further instructions.



ime in priimek:

vpisna št.:




Fakulteta za elektrotehniko, Univerza v Ljubljani

primeri števk: 0123456789

**1. test iz predmeta HAvOc (UNI)**

2.3.2011

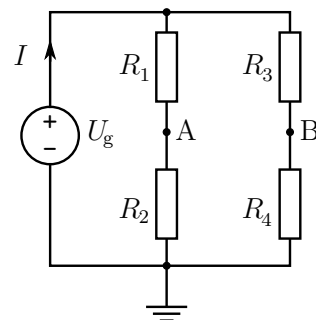1. Wheatstone bridge without null indicator has the following values of resistors:  $R_1 = 10 \Omega$ ,  $R_2 = 5 \Omega$ ,  $R_3 = 6 \Omega$  in  $R_4 = 4 \Omega$ . We have connected the bridge to a DC voltage source  $U = 1 \text{ V}$ .



- a) Determine the electric potential of junction B.

(A)  $V_B = 4 \text{ V}$                       (B)  $V_B \doteq 667 \text{ mV}$                       (C)  $V_B = 400 \text{ mV}$                       (D)  $V_B = 0 \text{ V}$


- b) What is the value of voltage  $U_{AB}$ ?

(A)  $U_{AB} \doteq 66.7 \text{ mV}$                       (B)  $U_{AB} = 500 \text{ mV}$                       (C)  $U_{AB} \doteq -66.7 \text{ mV}$                       (D)  $U_{AB} \doteq -267 \text{ mV}$

- c) Determine the current through resistor  $R_1$ .

(A)  $I \doteq 66.7 \text{ mA}$                       (B)  $I = 40 \text{ mA}$                       (C)  $I = 25 \text{ A}$                       (D)  $I \doteq 174 \text{ mA}$

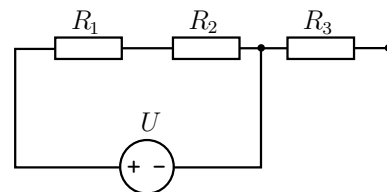2. The circuit is made of three resistors:  $R_1 = 10 \Omega$ ,  $R_2 = 5 \Omega$  in  $R_3 = 7 \Omega$ . Voltage source is  $U = 10 \text{ V}$ .



- a) What is the sum voltage on resistors  $R_1$  and  $R_2$ ?

(A)  $U_{R_1+R_2} = 20 \text{ V}$                       (B)  $U_{R_1+R_2} = 150 \text{ V}$                       (C)  $U_{R_1+R_2} = 10 \text{ V}$                       (D)  $U_{R_1+R_2} \doteq 4.67 \text{ V}$

- b) How much is the voltage on resistor  $R_3$ ?

(A)  $U_{R_3} = 5 \text{ V}$                       (B)  $U_{R_3} = 0 \text{ V}$                       (C)  $U_{R_3} \doteq 1.43 \text{ V}$                       (D)  $U_{R_3} = 10 \text{ V}$


- c) Determine the current through  $R_2$ !

(A)  $I = 0 \text{ A}$                       (B)  $I = 70 \text{ A}$                       (C)  $I \doteq 455 \text{ mA}$                       (D)  $I \doteq 667 \text{ mA}$

3. The entropy of isolated thermodynamical system

(A) can only increase.                      (B) can only decrease.                      (C) is always zero.                      (D) is always positive constant.

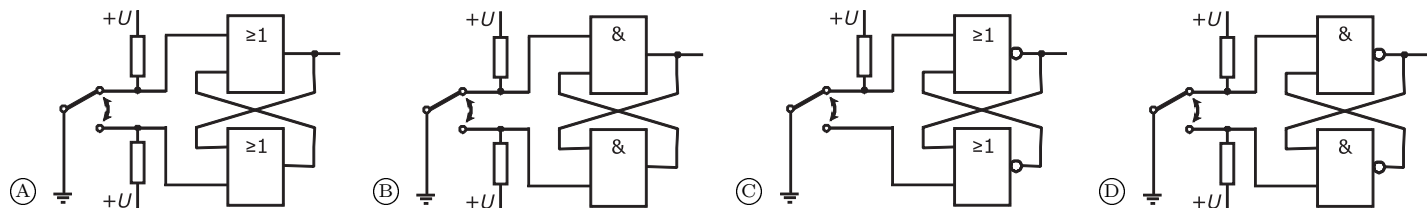4. Which circuits represents debounced switch?



This row can be used for further instructions.